

**UNIVERSITY OF SASKATCHEWAN**  
**MIDTERM EXAMINATION**

**EE 402.3      Microwave Engineering**


Professor: Dr. D. M. Klymyshyn

February 28, 2006

Time: **80 minutes**

Notes: One page formula sheet is allowed.  
Class data sheets are allowed.  
All 3 questions are of equal value.  
Assume all transmission lines are lossless.

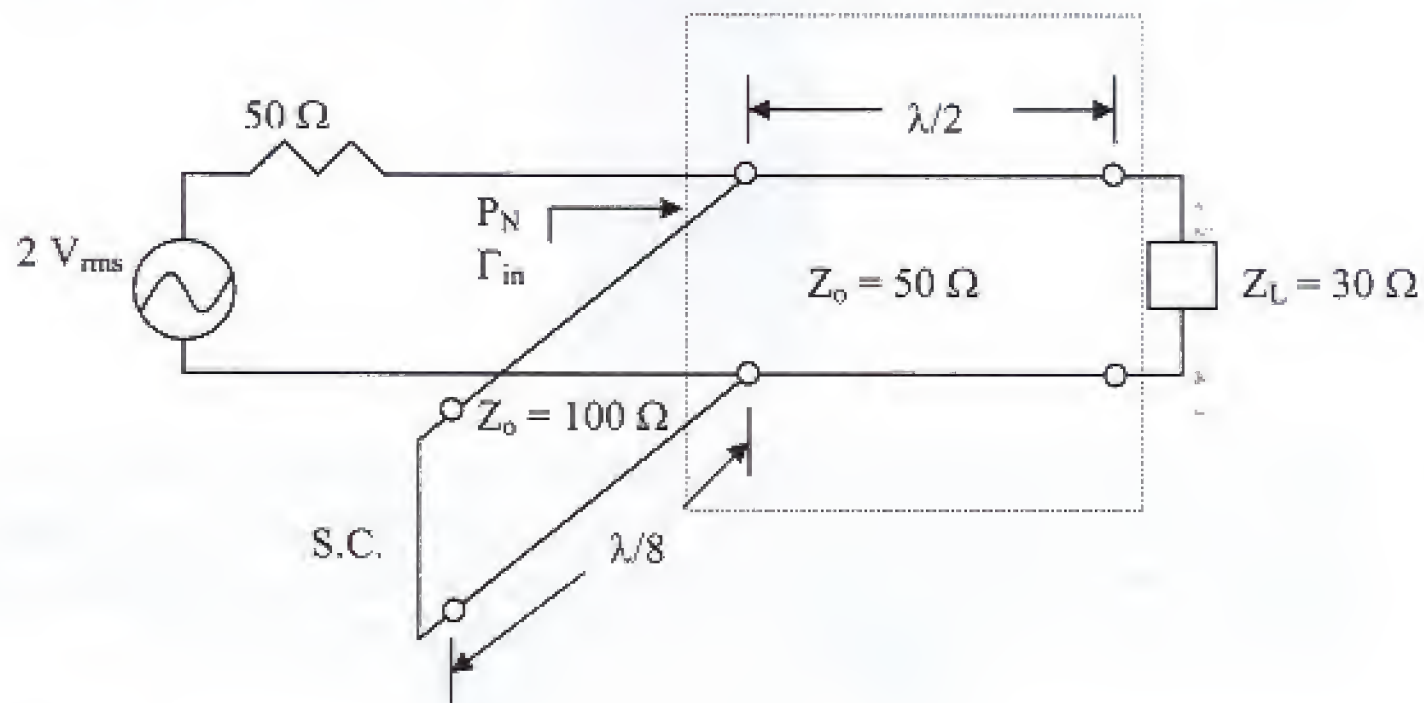1. A microwave circuit is shown. Using **equations** (not the Smith Chart), find the following:
- [S] parameters measured in a  $50\ \Omega$  system of the equivalent 2-port network highlighted in the dotted box (see Hints below).
  - Power **available** from the source ( $P_{avs}$ ).
  - Power delivered to the **network** ( $P_N$ ). Is  $\Gamma_{in} = S_{11}$ ? Explain.



**Hints:**

ABCD of Shunt Admittance ( $Y$ )


$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

ABCD of Lossless Trans. Line ( $Z_0, \beta, l$ )

$$\begin{bmatrix} \cos \beta l & jZ_0 \sin \beta l \\ jY_0 \sin \beta l & \cos \beta l \end{bmatrix}$$

2. Use the **Combined Smith Chart** provided and determine the length,  $l$ , of transmission line required on the input to make the input impedance of the following circuit **purely real** and as **large as possible**. Include the Smith Chart with your solution, clearly marking the construction using the "letters" given in the circuit and "arrows" to indicate the direction of your transformations. (Note: shunt elements shown are impedances)

a. What is  $Z_{in}$ ?

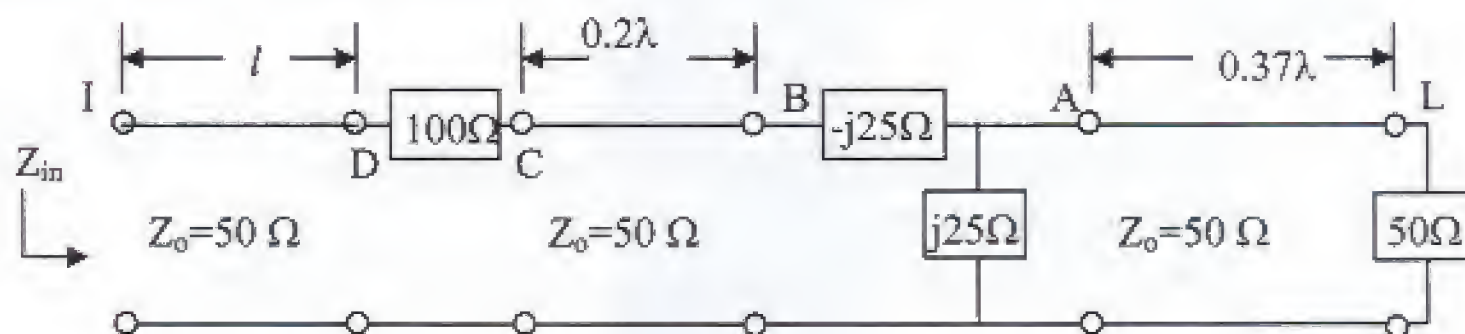

3. Design an **open circuit single shunt** stub tuner to transform a  $50\Omega$  load in a  $50\Omega$  system to an impedance of  $100 + j50\Omega$ . The stub should be as **short as possible**. Use  $50\Omega$  transmission lines for the tuner. Include the **Regular Smith Chart** provided with your solution, **clearly** marking all constructions.